

# Digital Logic Circuits

## 'Common Combinational Circuits'

ELEC2200  
Summer 2009

David J. Broderick  
[brodedj@auburn.edu](mailto:brodedj@auburn.edu)  
<http://www.auburn.edu/~brodedj>  
Office: Broun 360



# Design Validation

- Design is an important but small part of our jobs
- Before design is completed
  - Development of requirements
- After design is completed
  - Design Validation
  - Documentation of work



# Design Validation

- 800 people designed Pentium 4
  - Documentation is important!
- Insufficient design verification
  - Design error in floating-point division in Pentium processor in mid-1990's
  - Intel recalled 5 million devices
  - Cost: \$500,000,000
- **Check your answers**



# Hardware Description Languages

- Netlist (ASL)
  - Connections via signal name
- Schematic
  - Connections either explicit or via signal name
  - Produces a netlist for simulation
- Higher level language (VHDL or Verilog)
  - Synthesis to gate level netlist
- All of these result in design descriptions that can be used for simulation



# AUSIM

- Netlist description of design
- 4 files involved in a design
  - Input:
    - example.asl – netlist for design
    - example.vec – simulation input vectors
  - Output:
    - example.aud – analysis results
    - example.out – output of simulation




# ASL

- Hardware Description Language (Netlist)
- example.asl:

```
ckt: MUX in: A B S out: Z ;
```

 Notice:  
circuit name  
inputs  
outputs  
spaces




# ASL

- Hardware Description Language (Netlist)
- example.asl:

```
ckt: MUX in: A B S out: Z ;  
not: G1 in: S out: SN ;
```

 Notice:  
gate type  
gate name  
inputs  
outputs




# ASL

- Hardware Description Language (Netlist)
- example.asl:

```
ckt: MUX in: A B S out: Z ;  
not: G1 in: S out: SN ;  
and: G2 in: A SN out: G2 ;  
and: G3 in: S B out: G3 ;  
or: G4 in: G2 G3 out: Z ;
```

Notice:  
Output signal name matches

 



# VEC


- Each line is one input combination
- Order of inputs from example.asl preserved
- Lines starting with '#' are comments and transferred verbatim to the output file



# VEC

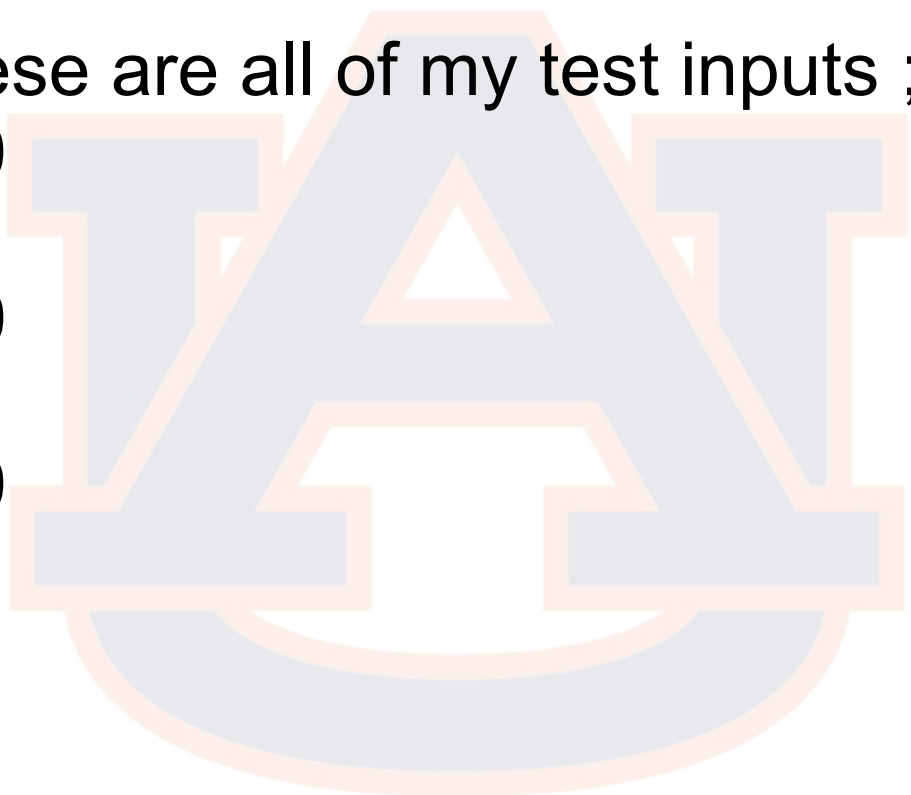- example.vec:

```
# These are all of my test inputs ;  
000  
001  
010  
011  
100  
101  
110  
111
```



- This is a natural order for test vectors but not required



# OUT

- example.out:

```
# ABS Z ;
```

```
# These are all of my test inputs ;
```

```
000 0
```

```
001 0
```

```
010 0
```

```
011 1
```

```
100 1
```

```
101 0
```

```
110 1
```

```
111 1
```

- Similar to .vec file
- Are outputs what we expected?




# AUD

- Analysis Results
- Contains all 4 metrics
  - # of gates
  - # of inputs/outputs
  - $G_{del}$  through worst case path
  - $P_{del}$  through worst case path
- Let's take a look...


 
# Subcircuits

- Modular design makes things faster
- Let's take our 2-to-1 MUX and build a 4-to-1 MUX




# Subcircuits

- A 4-to-1 MUX
- MUX4.asl:

```
subckt: MUX in: A B S out: Z ;  
not: G1 in: S out: SN ;  
and: G2 in: A SN out: G2 ;  
and: G3 in: S B out: G3 ;  
or: G4 in: G2 G3 out: Z ;
```

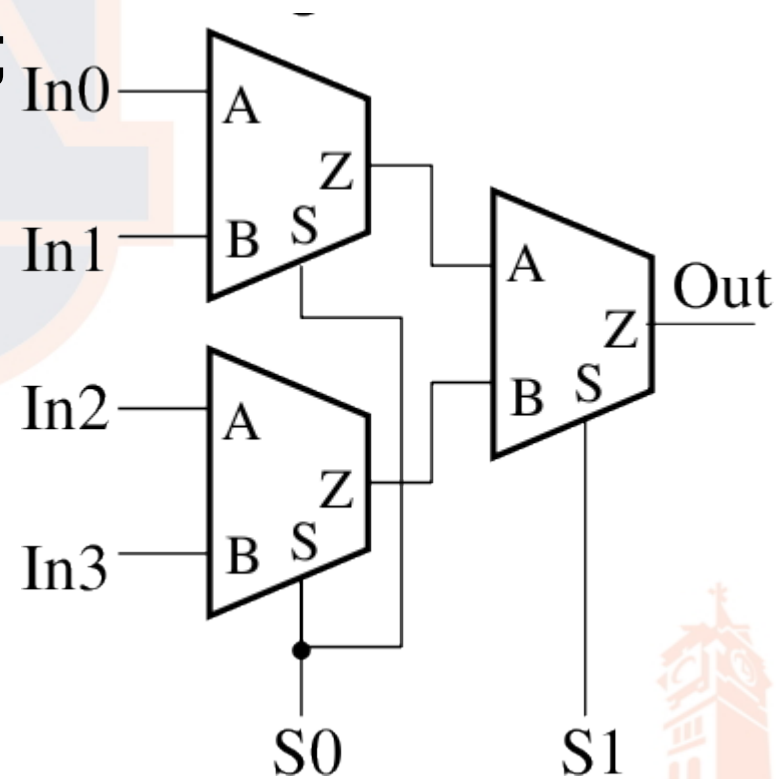- Subcircuit taken from our previous example



# Subcircuits

- A 4-to-1 MUX

- MUX4.asl:

```
subckt: MUX in: A B S out: Z ;
```


```
not: G1 in: S out: SN ;
```

```
and: G2 in: A SN out: G2 ;
```

```
and: G3 in: S B out: G3 ;
```

```
or: G4 in: G2 G3 out: Z ;
```

 
- Subcircuit taken from our previous example


 
# Subcircuits

- A 4-to-1 MUX
- MUX4.asl:

```
subckt: MUX in: A B S out: Z ;  
not: G1 in: S out: SN ;  
and: G2 in: A SN out: G2 ;  
and: G3 in: S B out: G3 ;  
or: G4 in: G2 G3 out: Z ;  
ckt: MUX4 in: In[0:3] S[0:1] out: Out ;  
MUX: M1 in: In0 In1 S0 out: M1 ;  
MUX: M2 in: In2 In3 S0 out: M2 ;  
MUX: M3 in: M1 M2 S1 out: Out ;
```





# Validation of MUX4

- MUX4.vec:
- Could use natural order of vectors 000000 to 111111
- Could also group vectors to ease validation



# Timing Issues

- AUSIM validates steady-state behavior well
- Transient errors also possible
- Delays differ through various paths, can lead to timing hazards (AKA glitches)
  - Static-1 hazard: produces a glitch to logic 0
  - Static-0 hazard: produces a glitch to logic 1



# Static Hazards

- Static-1 Hazard caused by a pair of inputs that:
  - Are logically adjacent
  - Both produce an output of 1
  - Cause a momentary logic 0 (called a 0 glitch) during a transition from one input value to the other
- Static-0 Hazard caused by a pair of inputs that:
  - Are logically adjacent
  - Both produce an output of 0
  - Cause a momentary logic 1 (called a 1 glitch) during a transition from one input value to the other




# Static Hazards

- Important properties:
  - A properly designed 2-level AND-OR (SOP) circuit has no static-0 hazards, but may have static-1 hazards
  - A properly designed 2-level OR-AND (POS) circuit has no static-1 hazards, but may have static-0 hazards




# Static Hazard Example

Multiplexer logic diagram

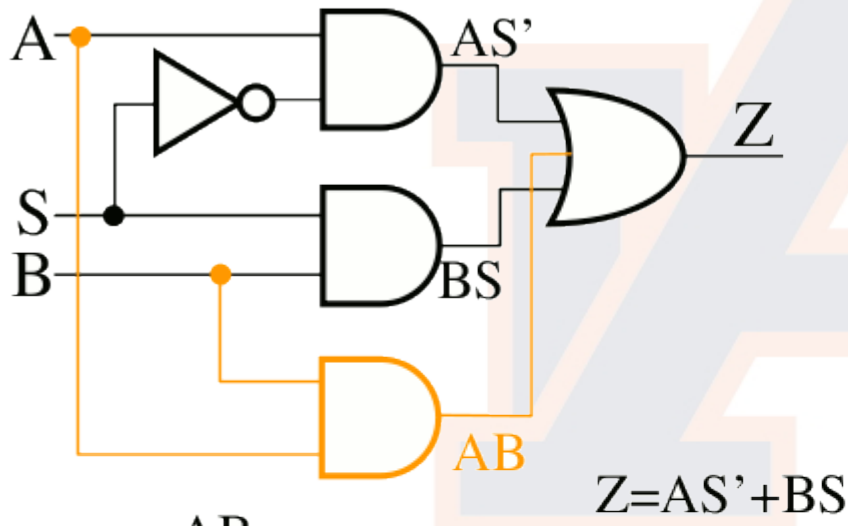

Timing diagram

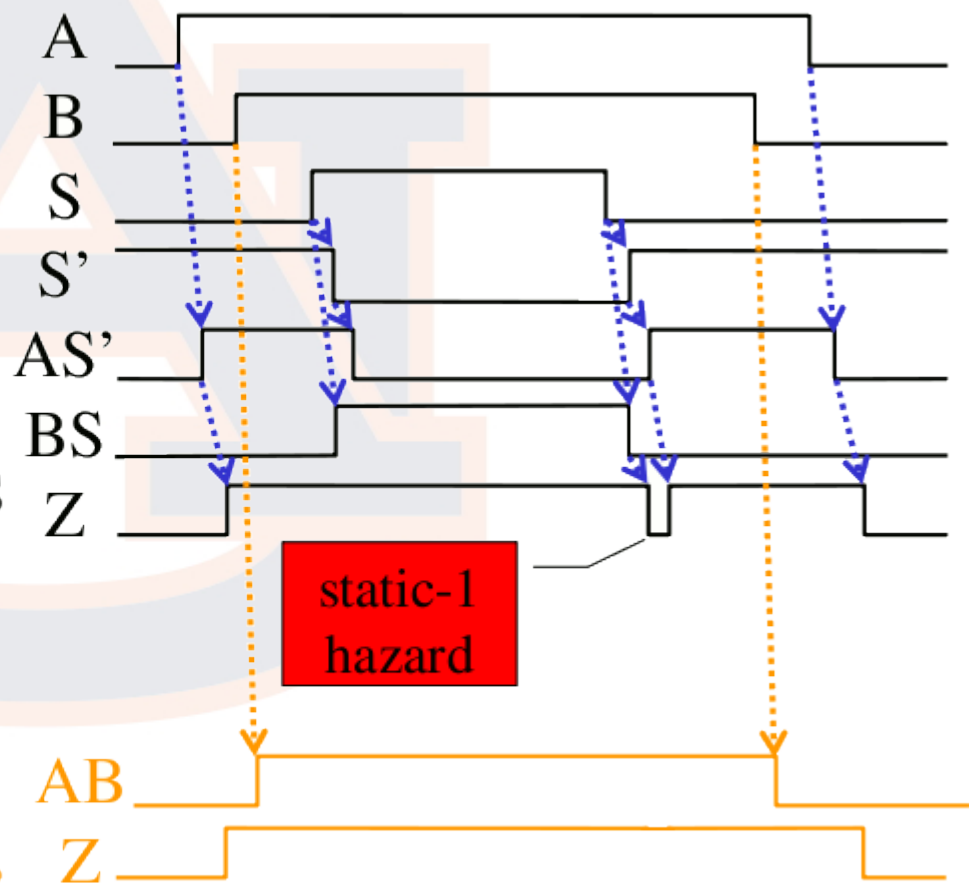

S \ AB	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$Z = AS' + BS + AB$

Note: this group removes hazard

Hazard-free multiplexer output

